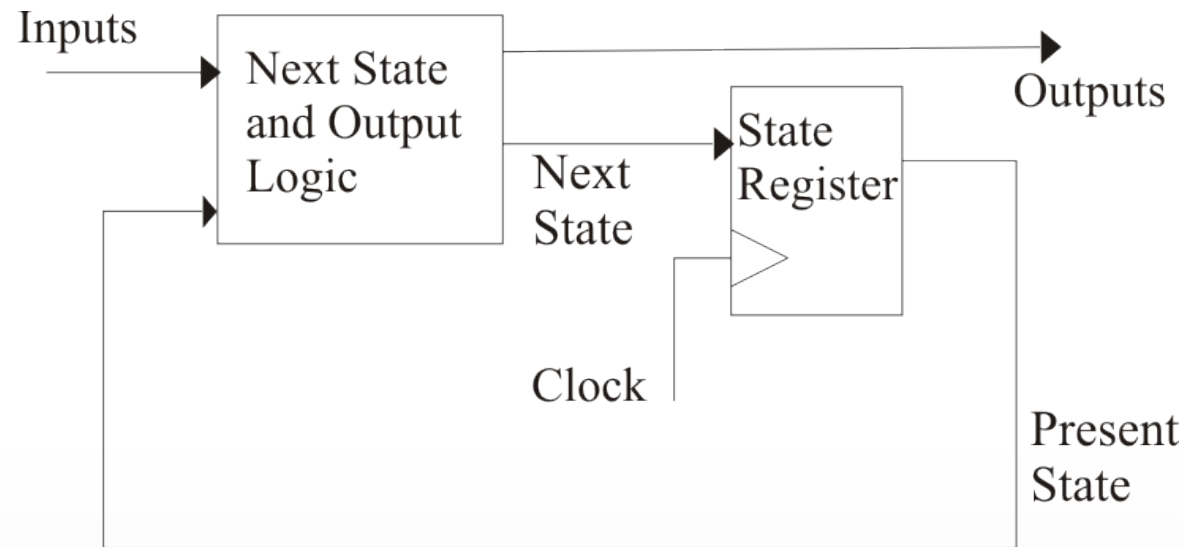


6. SystemVerilog for Sequential Design (2)

6.1 State Machines

SystemVerilog Model of State Machine




- SystemVerilog describes concurrent hardware
 - Each always block describes a piece of hardware
 - Therefore we can have more than one always block in a module
 - This model has one combinational block (Next State and Output) and one sequential (State Register)

SystemVerilog Model of State Machine

- Use an enumerated type for the states
 - Don't need to do a state assignment
- Combinational part is modelled with `always_comb`
 - Assign to next state and to outputs
 - Case statement – one branch for each state
 - If statements in each branch for Mealy (conditional) outputs and for selecting next state
 - Default assignments to each output and next state at start, to avoid accidental memory
- Sequential part is modelled with `always_ff`
 - Just like a flip-flop

State Machine Example

- Traffic Light Controller

 

Lights can be:


Major Road Red
Minor Road Green

or:

Major Road Green
Minor Road Red

2 states

ASM Chart

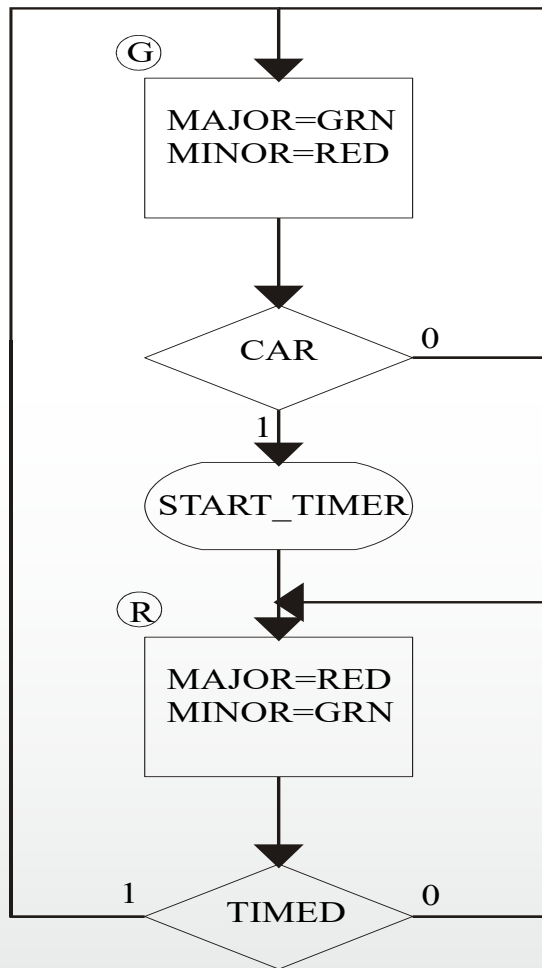

Two states (G and R)

Two inputs (CAR and TIMED)

Three outputs

(Minor=Green/Major=Red;
Major=Green/Minor=Red;
Start_timer)

```
module traffic (output logic start_timer,  
               major_green, minor_green,  
               input logic clock, n_reset, timed, car);  
  
enum {G, R} present_state, next_state;  
  
always_ff @(posedge clock, negedge n_reset)  
begin: SEQ //label  
    if (!n_reset)  
        present_state <= G;  
    else  
        present_state <= next_state;  
end
```

always_comb

begin: COM

start_timer = '0;

minor_green = '0;

major_green = '0;

next_state = present_state;

unique case (present_state)

G: **begin**

major_green = '1;

if (car)

begin

start_timer = '1;

next_state = R;

end

end

R: **begin**

minor_green = '1;

if (timed)

next_state = G;

end

endcase

end

endmodule

Comments

- present_state and next_state must be variables of enumerated type
- Care is needed with combinational process - can easily create latches - *BAD!*
 - Default values for outputs and next_state
- always blocks are labelled – need begin and end.
- unique case checks that all states are included
- There are other ways to do this, but this is recommended.

For you to do

- How would you build the timer? Can you find a suitable design from an earlier lecture?