
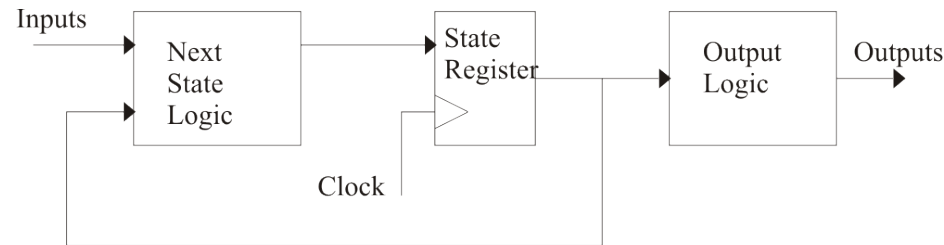


6.2 More State Machines

Other models

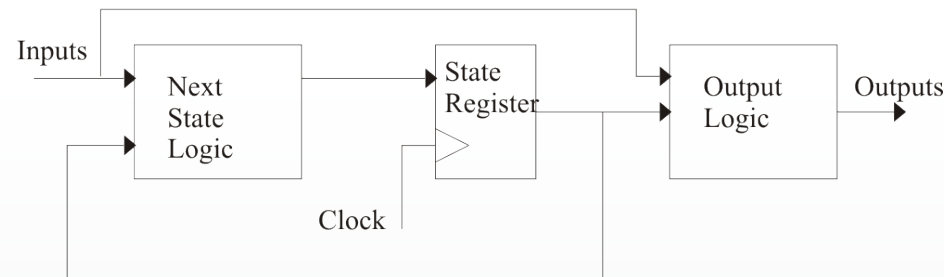

Moore Machine



Mealy Machine

- Separate always_comb for Next State and Output
- One always_ff for everything (but outputs will be flip-flops!)

Version 2 of Traffic Light Controller

```
enum {G, R} state;
always_ff @(posedge clock,
           negedge n_reset)
begin: SEQ
  if (!n_reset)
    state <= G;
  else
    unique case (state)
      G:  if (car)
            state <= R;
      R:  if (timed)
            state <= G;
    endcase
end
```


```
always_comb
begin: OP
  start_timer = '0;
  minor_green = '0;
  major_green = '0;
  unique case (state)
    G: begin
        major_green = '1;
        if (car)
          start_timer = '1;
        end
    R:
        minor_green = '1;
    endcase
  end
endmodule
```

Comments on version 2

- Next state logic is included with state registers
 - (Not Mealy or Moore)
- Works on all synthesis tools
- Some duplication of structure in the code

Vending Machine

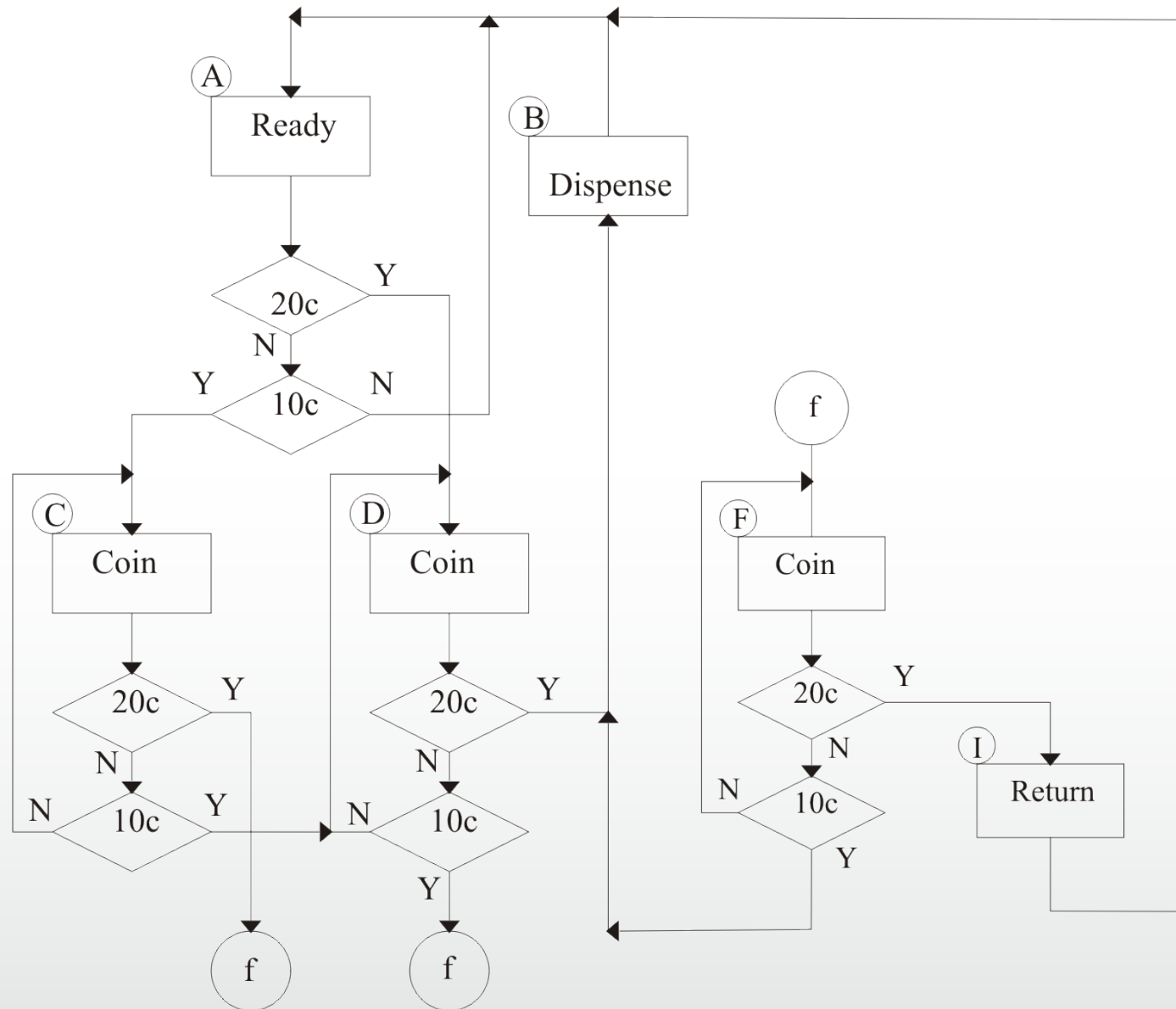- A drink costs 40c. (Euro cents.) The machine accepts 20c and 10c coins (all other coins are rejected by the mechanics of the system).
- Once 40c have been inserted, the drink is dispensed. If more than 40c are inserted, all coins are returned.
- The machine has two lights: one to show that it is ready for the next transaction, and one to show that further coins need to be inserted.



```
module vending(output logic ready,dispense,ret,coin
               input logic clock,n_reset,twenty,ten);

    enum {A, B, C, D, F, I} present_state, next_state;

always_ff @(posedge clock, negedge n_reset)
begin: SEQ
    if (~n_reset)
        present_state <= A;
    else
        present_state <= next_state;
end
```

```
always_comb
begin: COM
ready = '0;
dispense = '0;
ret = '0;
coin = '0;
unique case (present_state)
  A : begin
    ready = '1;
    if (twenty)
      next_state = D;
    else if (ten)
      next_state = C;
    else
      next_state = A;
    end
  B : begin
    dispense = '1;
    next_state = A;
    end
  C : begin
    coin = '1;
    if (twenty)
      next_state = F;
    else if (ten)
      next_state = D;
    else
      next_state = C;
    end
```

```
  D : begin
    coin = '1;
    if (twenty)
      next_state = B;
    else if (ten)
      next_state = F;
    else
      next_state = D;
    end
  F : begin
    coin = '1;
    if (twenty)
      next_state = I;
    else if (ten)
      next_state = B;
    else
      next_state = F;
    end
  I : begin
    ret = '1;
    next_state = A;
    end
endcase
end
endmodule
```


For you to do

- Rewrite the traffic light controller to use a single `always_ff` block (and no `always_comb` blocks).
 - Why does this behave a little differently to the other versions?